

FIG. 2.180
Problem 37.

2.8 Clippers

38. Determine v_o for each network of Fig. 2.181 for the input shown.



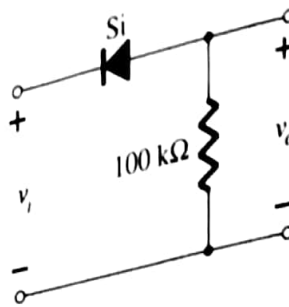
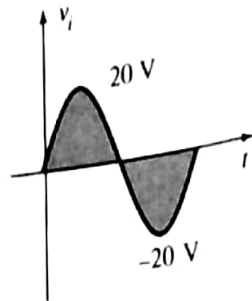
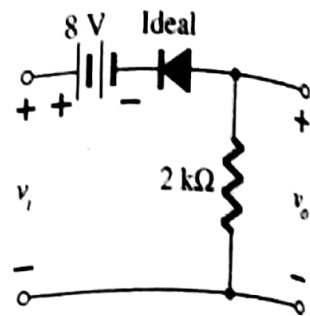



FIG. 2.181
Problem 38.

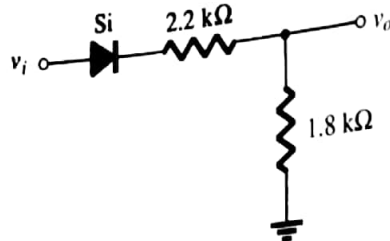

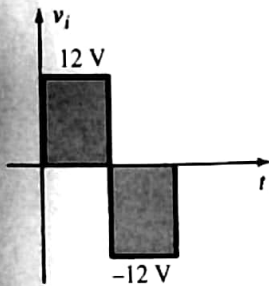39. Determine v_o for each network of Fig. 2.182 for the input shown.





(a)

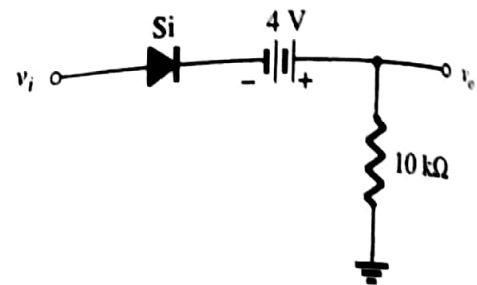


(b)

FIG. 2.182
Problem 39.

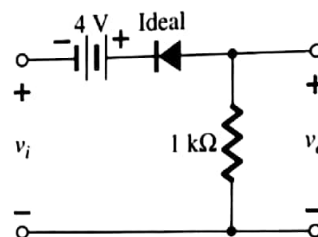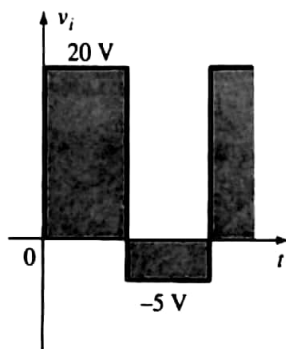- *40. Determine v_o for each network of Fig. 2.183 for the input shown.



(a)

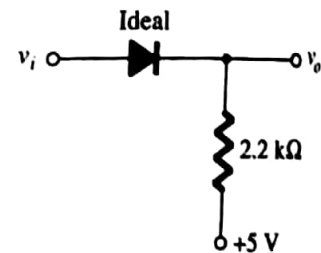

(b)

FIG. 2.183
Problem 40.